



VLSI Design (BEC-41) **(Unit- 2, Lecture- 9)**



Presented By:
Prof. R. K. Chauhan

Department of Electronics and Communication Engineering



Problem 1: Design following Boolean expression using complementary CMOS and Pseudo NMOS logic:

$$Y = \overline{AB + C(A + D)} \quad Y = AB + BC + D.$$

 


Fig. using complementary CMOS logic


 


Fig. using Pseudo NMOS logic

 

Problem 2: Realized following Boolean function and find $(W/L)_n$ equivalent and $(W/L)_p$ equivalent, if $(W/L)_n=10$ and $(W/L)_p=15$:

$$Y = \overline{(D + E + A)(B + C)}$$



$$\begin{aligned} \left(\frac{W}{L}\right)_{n,eq} &= \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E + \left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_B + \left(\frac{W}{L}\right)_C}} \\ &= \frac{1}{\frac{1}{30} + \frac{1}{20}} = 12 \end{aligned}$$


$$\begin{aligned} \left(\frac{W}{L}\right)_{p,eq} &= \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_D} + \frac{1}{\left(\frac{W}{L}\right)_E} + \frac{1}{\left(\frac{W}{L}\right)_A}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_C}} \\ &= \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15}} + \frac{1}{\frac{1}{15} + \frac{1}{15}} = 12.5 \end{aligned}$$



Problem 2:

A. Identify the worst-case input combination(s) for V_{OL} .

B. Calculate the worst-case value of V_{OL} . (Assume that all pull-down transistors have the same body bias and initially, that $V_{OL} = 5\% V_{DD}$.)

 



Solution 2:

Class1: A-C

Class1: B-D

Class1: B-E

Class2: B-D-E

Class3: A-C-B-D-E

$$V_{OL1} > V_{OL2} > V_{OL3}$$

Hence worst case V_{OL} in class 1 combination.

$$\text{Given: } R_n / (R_u + R_n) \cdot V_{DD} = 5\% V_{DD} = V_{DD} / 20$$

$$\text{Hence } 19R_n = R_u$$

$$\text{For Class1: } V_{OL} = 2R_n / (R_u + 2R_n) \cdot V_{DD}$$


$$V_{OL} = V_{DD} / 10.5$$



Problem 3: Find the effective output node capacitance in both two cases of given figure:

A. The input V_A is equal to V_{OH} and the other input V is switching from V_{OH} to V_{OL} .

B. V_B is equal to V_{OH} and V_A switches from V_{OH} to V_{OL} .

 



Solution 3:

- The input V_A is equal to V_{OH} and the other input V is switching from V_{OH} to V_{OL} . In this case, both the output voltage V_{OUT} , and the internal node voltage V_x will rise, resulting in:

$$C_{load} = C_{gd,load} + C_{gd,A} + C_{gd,B} + C_{gs,A} \\ + C_{db,A} + C_{db,B} + C_{sb,A} + C_{sb,load} + C_{wire}$$

- Note that this value is quite conservative and fully reflects the internal node capacitances into the lumped output capacitance C_{load} in reality, only a fraction of the internal node capacitance is reflected into C_{load} .
- Now consider another case where V_B is equal to V_{OH} and V_A switches from V_{OH} to V_{OL} . In this case, the output voltage V_{out} , will rise, but the internal node voltage V_x , will remain low because the bottom driver transistor is on. Thus, the lumped output capacitance is

$$C_{load} = C_{gd,load} + C_{gd,A} + C_{db,A} + C_{sb,load} + C_{wire}$$