



Control Systems

Subject Code: BEC-26

Third Year ECE

Unit-I

Shadab A. Siddique
Assistant Professor

Maj. G. S. Tripathi
Associate Professor



Lecture 8

Department of Electronics & Communication Engineering,
Madan Mohan Malaviya University of Technology, Gorakhpur




UNIT- I

- Introduction to Control system
 - ❖ Control System – Definition and Practical Examples
 - ❖ Basic Components of a Control System
- Feedback Control Systems:
 - ❖ Feedback and its Effect
 - ❖ Types of Feedback Control Systems
- Block Diagrams:
 - ❖ Representation and reduction
 - ❖ Signal Flow Graphs
- **Modeling of Physical Systems:**
 - ❖ **Electrical Networks and Mechanical Systems**
 - ❖ Force-Voltage Analogy
 - ❖ Force-Current Analogy



Mathematic Modeling of Dynamical Systems

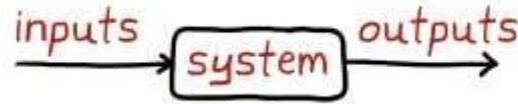

- The set of mathematical equation describing the dynamic characteristics of a system is called mathematical model of a system.
- Dynamics/ mathematical equation of many systems can be written in terms of differential equations
 - Mechanical, thermal, electrical, economic, biological systems etc.
- We said that these D.E.'s can be derived using basic physical laws
- All systems we will study will be 'causal', i.e. the system's response at any time 't' depends only on past and not future inputs
- Recall transfer functions:
 - It is the ratio of Laplace Transform of output to Laplace Transform of input, when initial conditions are zero.
 - We assume
 - Zero initial conditions
 - Linearity
 - Time Invariance



Similarities in Mechanical and Electrical Systems

3 basic components in mechanical systems:

- Mass
- Spring
- Damper

✓ 3 basic components in electrical systems:

- Resistance
- Capacitor
- Inductor

- Basic form of differential equations is the same.
- Therefore, learning to model one type of system easily leads to modeling method for the other.
- Also, electrical and mechanical systems can be easily cascaded in block diagrams due to this similarity.
- In fact, many other types of systems have similar forms
- We will begin with electrical systems. This will make modeling mech easier!

Modelling Electrical Systems (Nise)

- Current (i) is the rate of flow of charge (q)

$$i(t) = \frac{dq(t)}{dt} \Rightarrow q(t) = \int i(t) dt$$

- Taking Laplace transform

$$I(s) = sQ(s) \Rightarrow Q(s) = \frac{1}{s} I(s)$$

- Impedance (complex resistance) is defined as

$$z = \frac{v}{i} \Rightarrow Z(s) = \frac{V(s)}{I(s)}$$

- It's mathematical inverse is called admittance.



Passive Electric Components

- Resistor:

$$\triangleright v(t) = i(t)R = R \frac{dq(t)}{dt} \Rightarrow V(s) = I(s)R$$

$$\triangleright i(t) = \frac{v(t)}{R} \Rightarrow I(s) = \frac{V(s)}{R}$$

- Capacitor:

$$\triangleright v(t) = \frac{1}{C}q(t) = \frac{1}{C} \int i(t)dt \Rightarrow V(s) = \frac{1}{Cs}I(s)$$

$$\triangleright i(t) = C \frac{dv(t)}{dt} \Rightarrow I(s) = CsV(s)$$

- Inductor:

$$\triangleright v(t) = L \frac{di(t)}{dt} = L \frac{d^2q(t)}{dt^2} \Rightarrow V(s) = LsI(s)$$

$$\triangleright i(t) = \frac{1}{L} \int v(t)dt \Rightarrow I(s) = \frac{1}{Ls}V(s)$$

- We will combine these elements in complex networks using Kirchoff's Laws


– Current and Voltages in a loop sum to zeros

Component	Voltage-current	Current-voltage	Voltage-charge	Impedance $Z(s) = V(s)/I(s)$	Admittance $Y(s) = I(s)/V(s)$
 Capacitor	$v(t) = \frac{1}{C} \int_0^1 i(\tau)d\tau$	$i(t) = C \frac{dv(t)}{dt}$	$v(t) = \frac{1}{C}q(t)$	$\frac{1}{Cs}$	Cs
 Resistor	$v(t) = Ri(t)$	$i(t) = \frac{1}{R}v(t)$	$v(t) = R \frac{dq(t)}{dt}$	R	$\frac{1}{R} = G$
 Inductor	$v(t) = L \frac{di(t)}{dt}$	$i(t) = \frac{1}{L} \int_0^1 v(\tau)d\tau$	$v(t) = L \frac{d^2q(t)}{dt^2}$	Ls	$\frac{1}{Ls}$

Note: The following set of symbols and units is used throughout this book: $v(t)$ – V (volts), $i(t)$ – A (amps), $q(t)$ – Q (coulombs), C – F (farads), R – Ω (ohms), G – Ω (mhos), L – H (henries).

Single Loop RLC Circuit

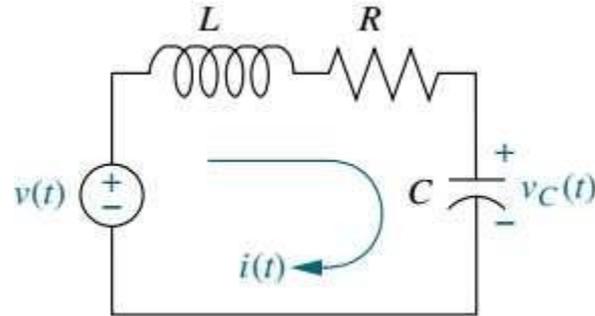- Find transfer function of $V_c(s)$ to input $V(s)$



Summing the voltages around the loop, assuming zero initial conditions, yields the integro-differential equation for this network as


$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$

Changing variables from current to charge using $i(t) = dq(t)/dt$ yields

$$L \frac{d^2q(t)}{dt^2} + R \frac{dq(t)}{dt} + \frac{1}{C} q(t) = v(t)$$

From the voltage-charge relationship for a capacitor


$$q(t) = Cv_C(t)$$

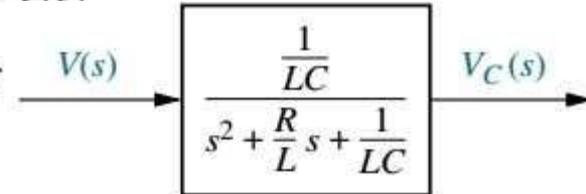


$$LC \frac{d^2v_C(t)}{dt^2} + RC \frac{dv_C(t)}{dt} + v_C(t) = v(t) \Rightarrow (LCs^2 + RCs + 1)V_C(s) = V(s)$$

Simplifying the Procedure

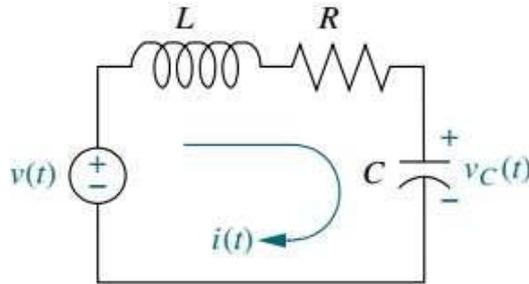- Let us look at this in another way.
 - Resistor: $V_R(s) = I(s)R$
 - Capacitor: $V_C(s) = \frac{1}{Cs}I(s)$
 - Inductor: $V_L(s) = LsI(s)$
- Let's define impedance (similar to resistance) as $Z(s) = \frac{V(s)}{I(s)}$
- Unlike resistance, impedance is also applicable to capacitors & inductors.
- It represents information about dynamic behavior of components.


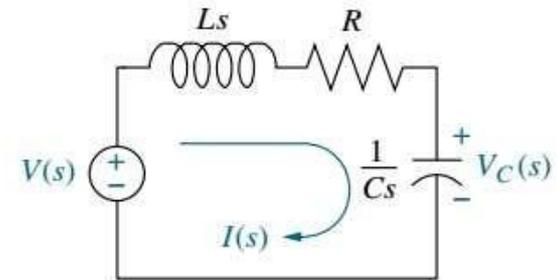
$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(t)$$




$$\left(Ls + R + \frac{1}{Cs} \right) I(s) = V(s)$$



[Sum of impedances] $I(s) =$ [Sum of applied voltages]


Solving Multi-Loop Electric Circuits

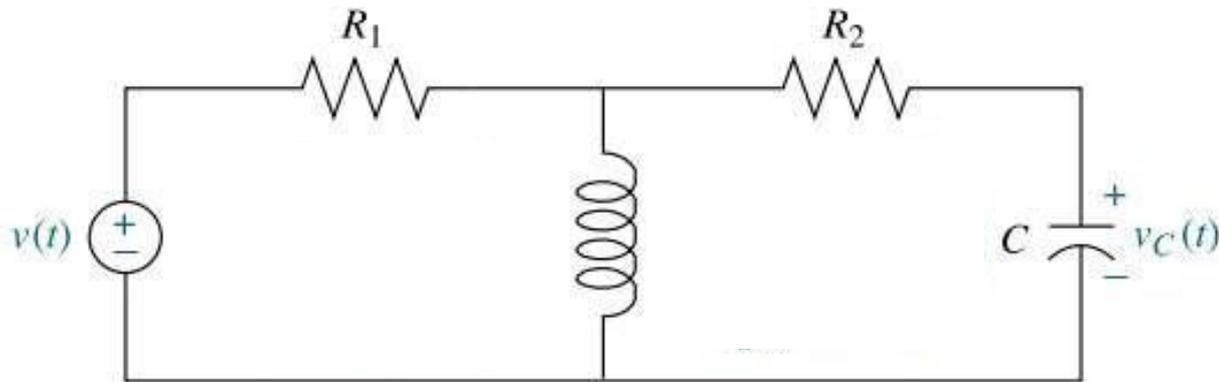- For multiple loops and loads, use the following recipe.
 - Replace passive element values with their impedances.
 - Replace all sources and time variables with their Laplace transform.
 - Assume a transform current and a current direction in each mesh.
 - Write Kirchoff's voltage law around each mesh.
 - Solve the simultaneous equations for the output.
 - Form the transfer function.



Multi-loop Example

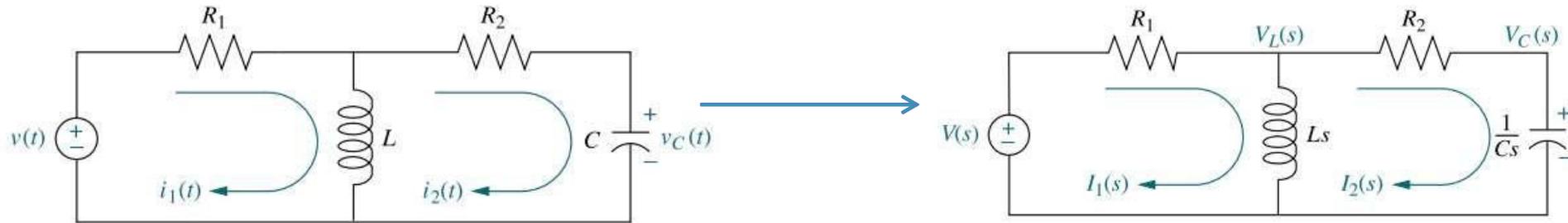- Find the transfer function $I_2(s) / V(s)$



- Solving for Loop 1 and Loop 2

$$(R_1 + Ls)I_1(s) - LsI_2(s) = V(s) \quad (1)$$

$$-LsI_1(s) + \left(Ls + R_2 + \frac{1}{Cs}\right)I_2(s) = 0 \quad (2)$$

- There are various ways to solve this.

$$\begin{bmatrix} R_1 + Ls & -Ls \\ -Ls & Ls + R_2 + 1/Cs \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} V(s) \\ 0 \end{bmatrix}$$

- This will yield the following transfer function

$$G(s) = \frac{I_2(s)}{V(s)} = \frac{Ls}{\Delta} = \frac{LCs^2}{(R_1 + R_2)LCs^2 + (R_1R_2C + L)s + R_1}$$



Summarizing the Method


- Let us look at the pattern in the last example

$$\begin{aligned} & \left[\begin{array}{c} \text{Sum of} \\ \text{impedances} \\ \text{around Mesh 1} \end{array} \right] I_1(s) - \left[\begin{array}{c} \text{Sum of} \\ \text{impedances} \\ \text{common to the} \\ \text{two meshes} \end{array} \right] I_2(s) = \left[\begin{array}{c} \text{Sum of applied} \\ \text{voltages around} \\ \text{Mesh 1} \end{array} \right] \\ - \left[\begin{array}{c} \text{Sum of} \\ \text{impedances} \\ \text{common to the} \\ \text{two meshes} \end{array} \right] I_1(s) + \left[\begin{array}{c} \text{Sum of} \\ \text{impedances} \\ \text{around Mesh 2} \end{array} \right] I_2(s) = \left[\begin{array}{c} \text{Sum of applied} \\ \text{voltages around} \\ \text{Mesh 2} \end{array} \right] \end{aligned}$$

- This form will help us write such equations rapidly
- Mechanical equations of motion (covered next) have the same form. So, this form is very useful!

Class Quiz

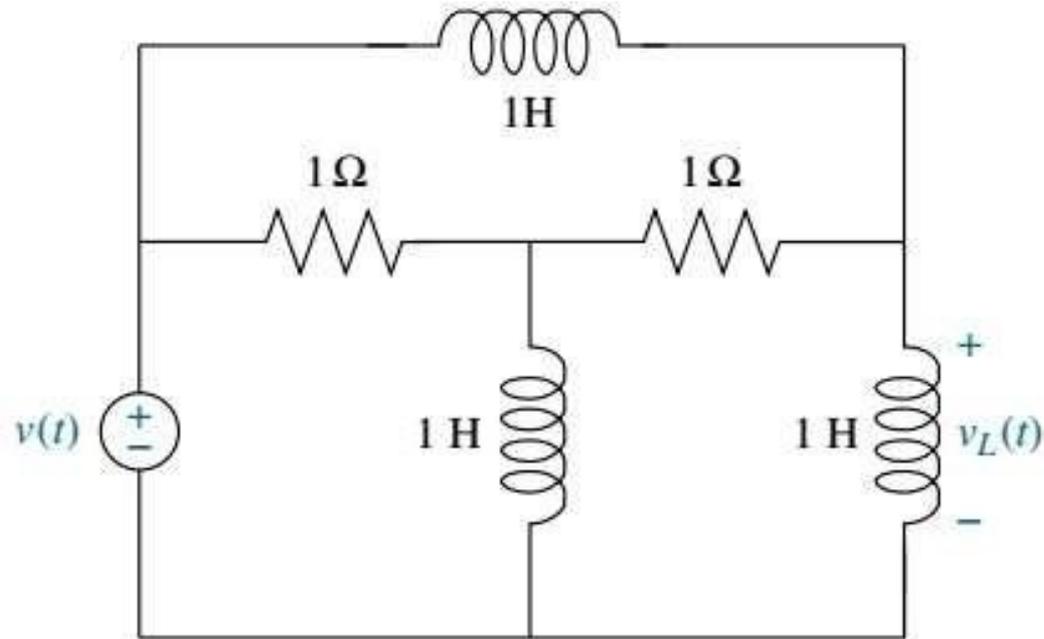PROBLEM: Find the transfer function, $G(s) = V_L(s)/V(s)$, for the circuit given



ANSWER: $V_L(s)/V(s) = (s^2 + 2s + 1)/(s^2 + 5s + 2)$

Mechanical Systems (Translational)

- Many concepts applied to electrical networks can also be applied to mechanical systems via analogies.
- This will also allow us to model hydraulic/pneumatic/thermal systems.


Component	Force-velocity	Force-displacement	Impedance $Z_M(s) = F(s)/X(s)$
<p>Spring</p>	$f(t) = K \int_0^t v(\tau) d\tau$	$f(t) = Kx(t)$	K
<p>Viscous damper</p>	$f(t) = f_v v(t)$	$f(t) = f_v \frac{dx(t)}{dt}$	$f_v s$
<p>Mass</p>	$f(t) = M \frac{dv(t)}{dt}$	$f(t) = M \frac{d^2 x(t)}{dt^2}$	Ms^2




Electrical/Mechanical Analogies

- Mechanical systems, like electrical networks, have 3 passive, linear components:
 - Two of them (spring and mass) are energy-storage elements; one of them, the viscous damper, dissipates energy.
 - The two energy-storage elements are analogous to the two electrical energy-storage elements, the inductor and capacitor. The energy dissipater is analogous to electrical resistance.
- Displacement 'x' is analogous to current I
- Force 'f' is analogous to voltage 'v'
- Impedance ($Z=V/I$) is therefore $Z=F/X$
- Since, [Sum of Impedances] $I(s) =$ [Sum of applied voltages]
- Hence, [Sum of Impedances] $X(s) =$ [Sum of applied forces]



Electric Mechanical Analogy

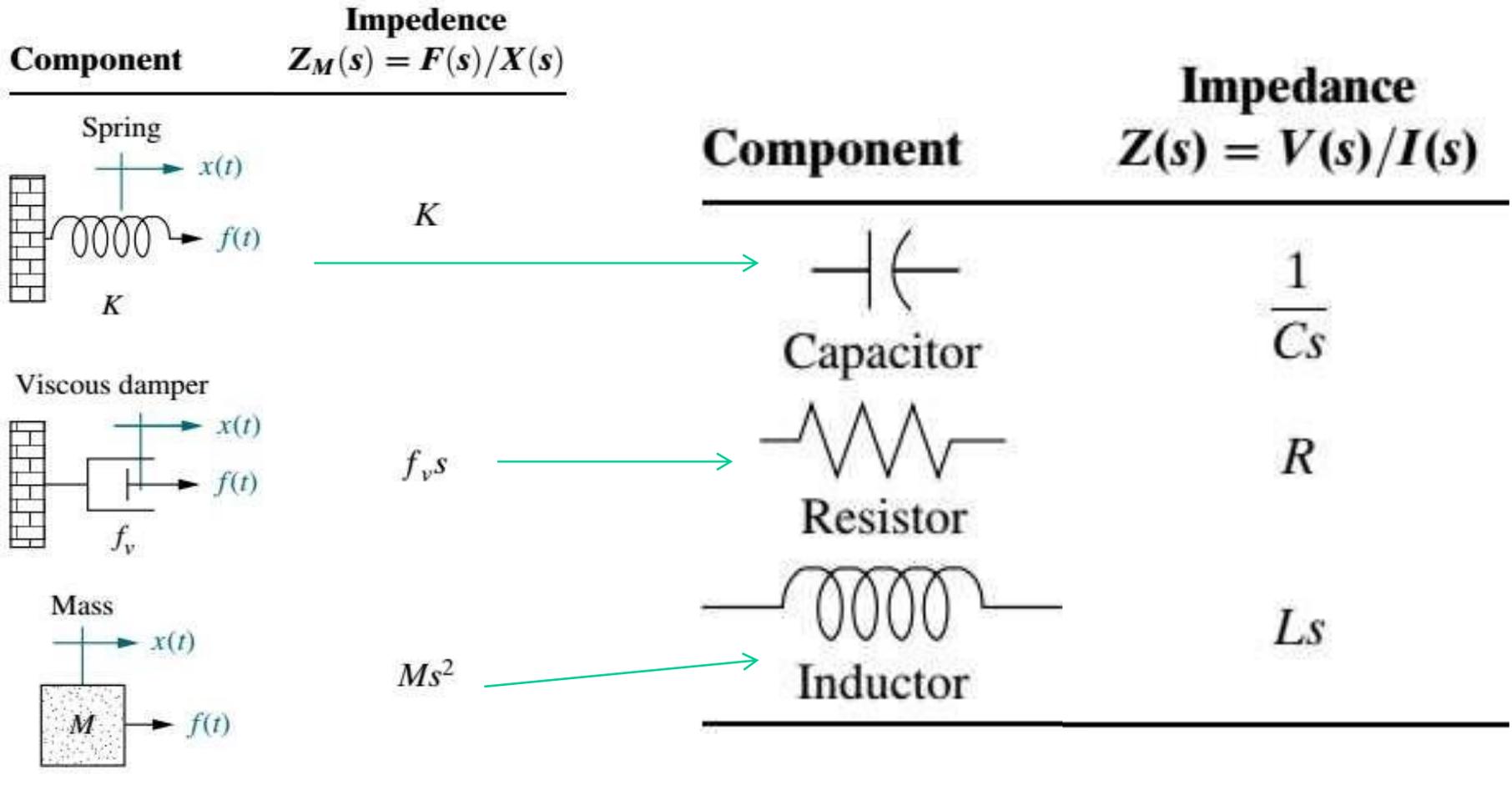

Spring Mass Damper System

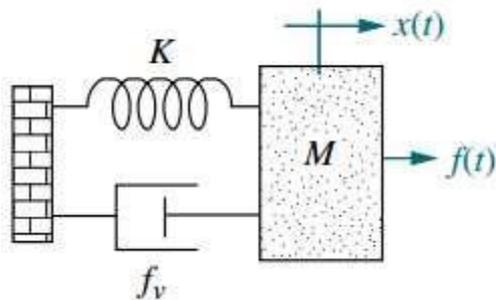

Find the transfer function, $X(s)/F(s)$

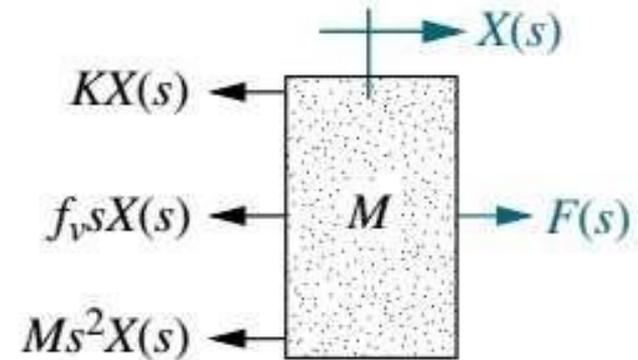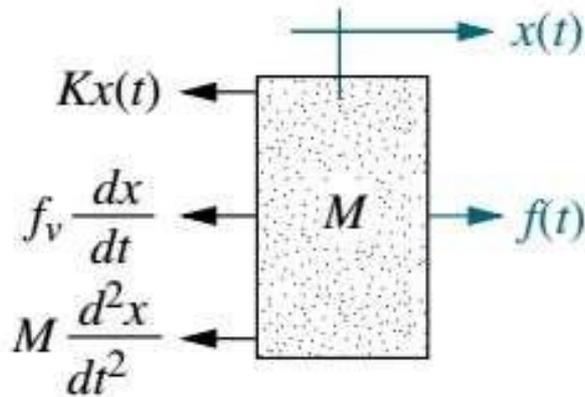

$$M \frac{d^2x(t)}{dt^2} + f_v \frac{dx(t)}{dt} + Kx(t) = f(t)$$


$$(Ms^2 + f_v s + K)X(s) = F(s)$$

Solving for the transfer function yields

$$G(s) = \frac{X(s)}{F(s)} = \frac{1}{Ms^2 + f_v s + K}$$

Transfer Function??

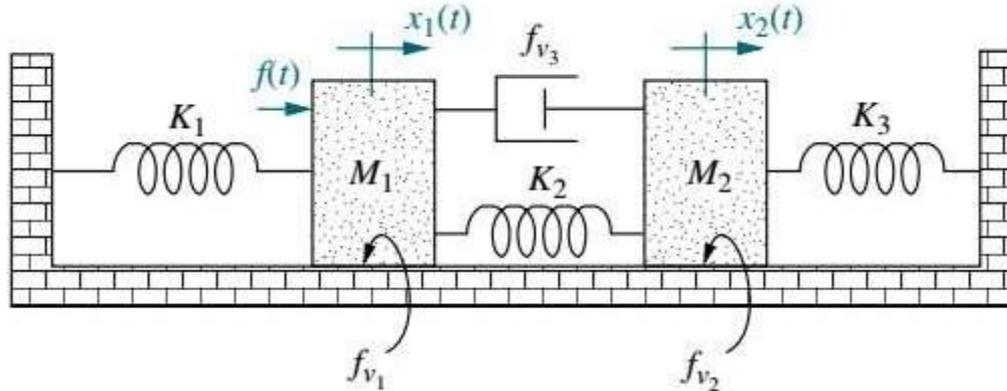Find the transfer function, $X_2(s)/F(s)$.



- System has two degrees of freedom, since each mass can be moved in the horizontal direction while the other is held still.
- 2 simultaneous equations of motion will be required to describe system.
- The two equations come from free-body diagrams of each mass.
- Forces on M_1 are due to (a) its own motion and (b) motion of M_2 transmitted to M_1 through the system.